

ASSIGNMENT-6

INTRODUCTION TO ELCTRICAL ENGINEERING

Professor- Dr. Neethu Mohan



Team Members

BATCH-A TEAM-7

GAJULA SRI VATSANKA CB.EN.U4AIE.21010

GUNNAM HIMAMSH CB.EN.U4AIE.21014

M.PRASANNA TEJA CB.EN.U4AIE.21032



VIKHYAT BANSAL CB.EN.U4AIE.21076

QUESTION


1. Implement the following circuits in Falstad circuit simulator. Also upload the files along with input/output waveforms.
 1. Inverting amplifier
 2. Non inverting amplifier
 3. Summing amplifier
 4. Difference amplifier
 5. Integrator
 6. Differentiator
 7. Inverting comparator
 8. Non inverting comparator
 9. Zero-crossing detector
 10. Schmitt Trigger
 11. Astable multivibrator
 12. Resistive-ladder DAC

1. Inverting Amplifier [\[LINK\]](#)

Circuit Diagram

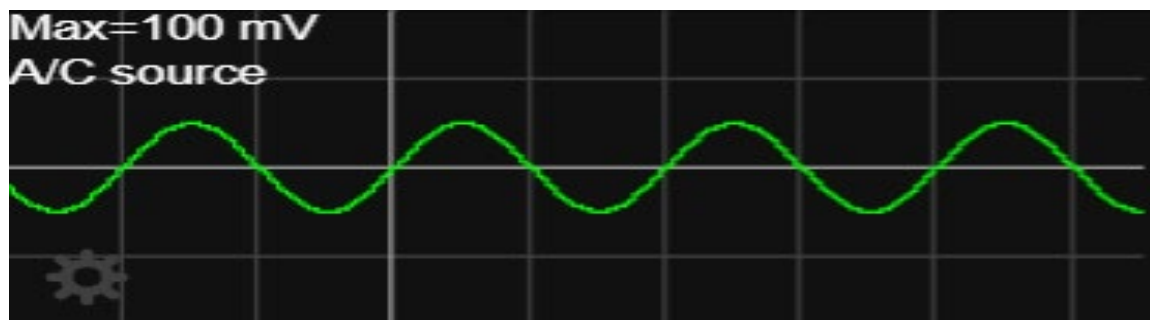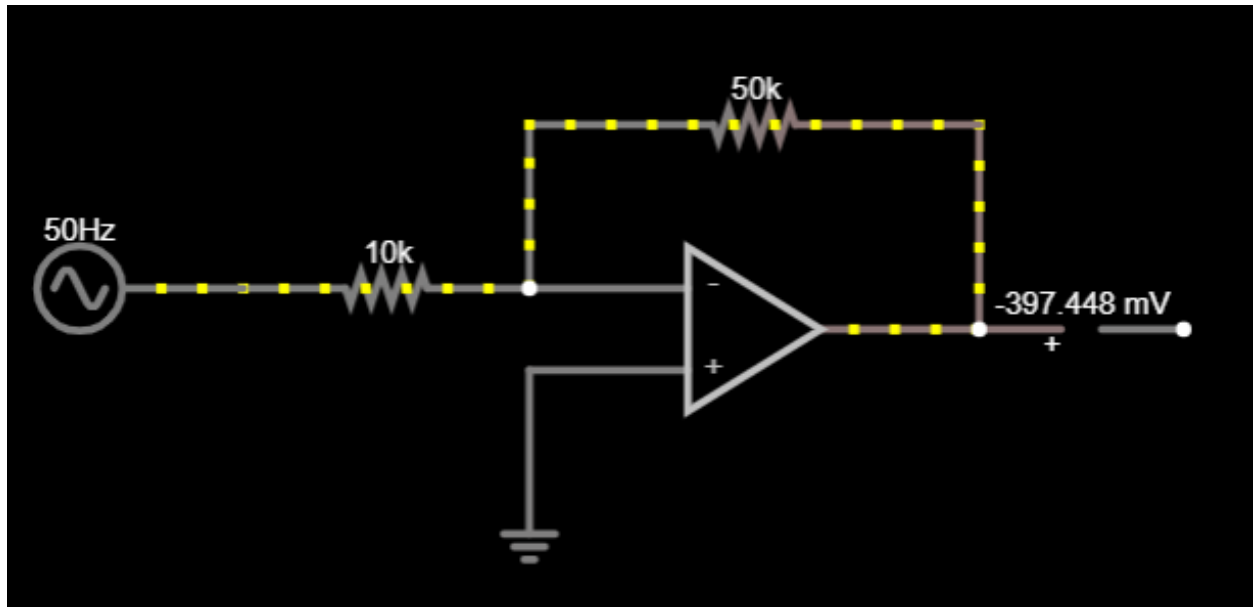


Output

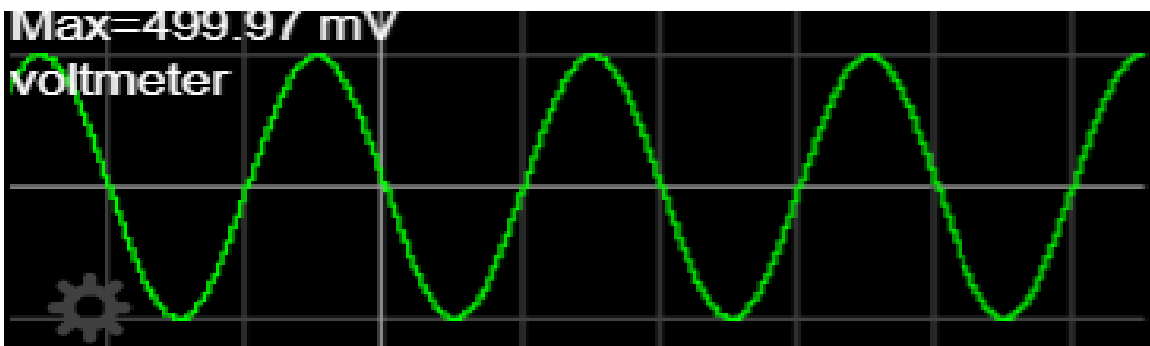


2. Non-Inverting Amplifier [\[LINK\]](#)


Circuit Diagram

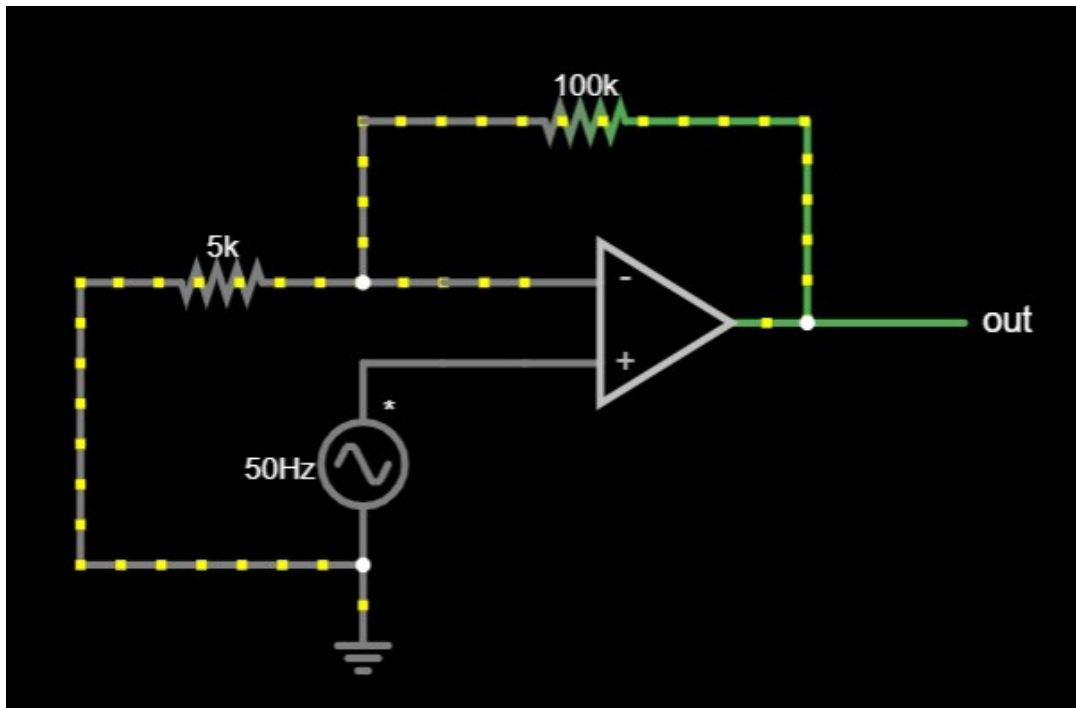

Input

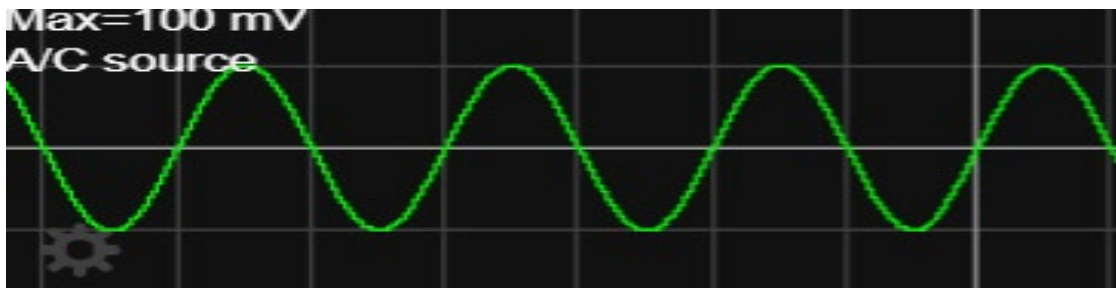


Output

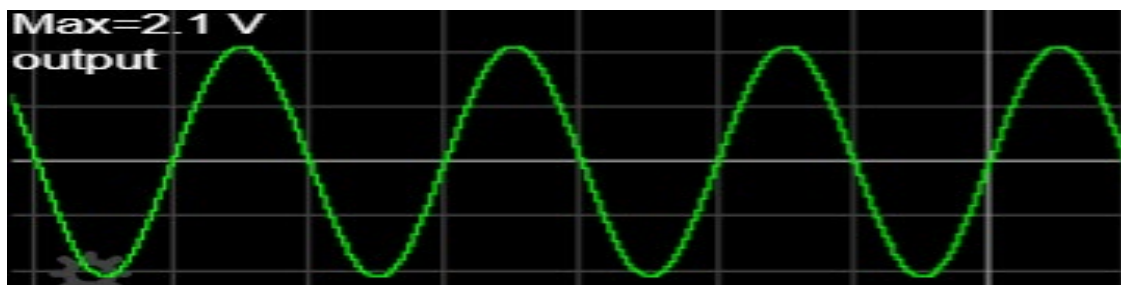


3. Summing Amplifier [\[LINK\]](#)


Circuit Diagram

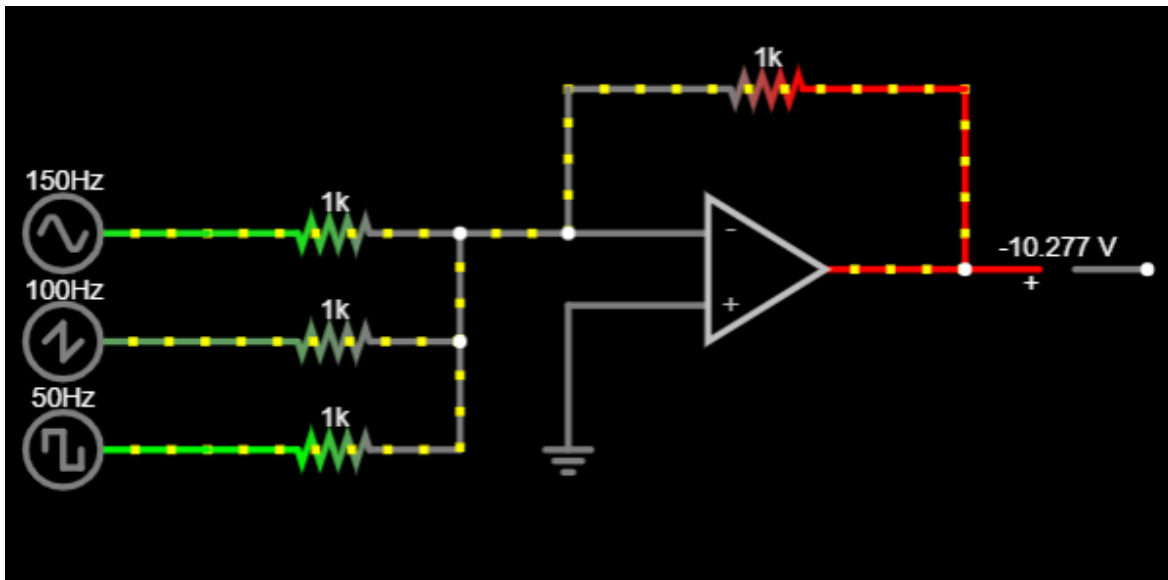

Input

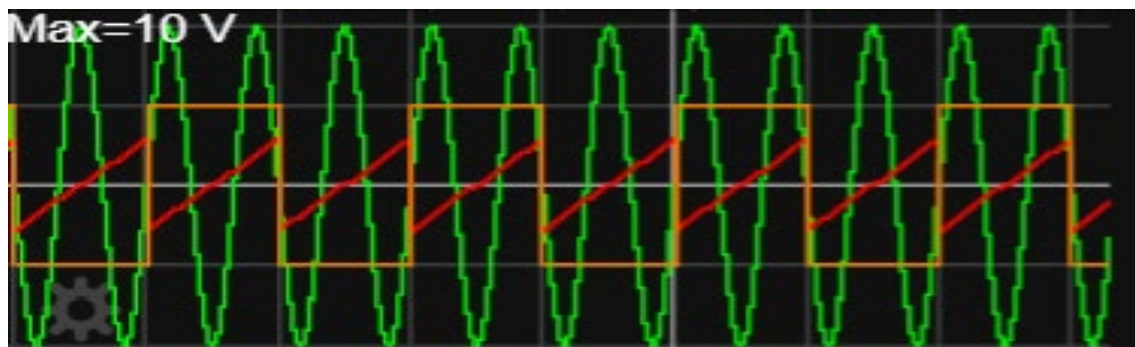


Output

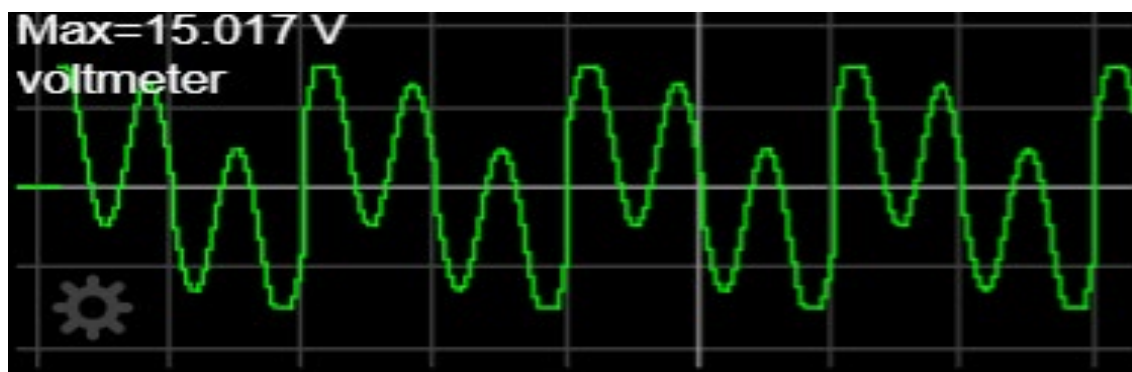


4. Difference Amplifier

Circuit Diagram

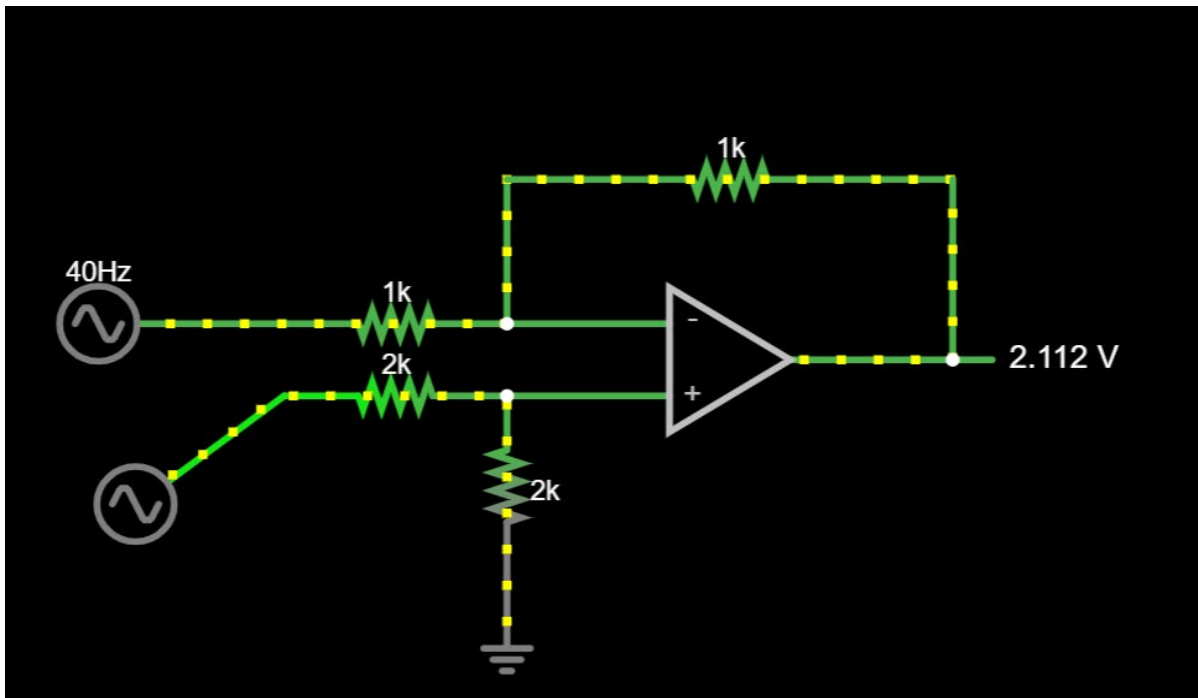


Input-1

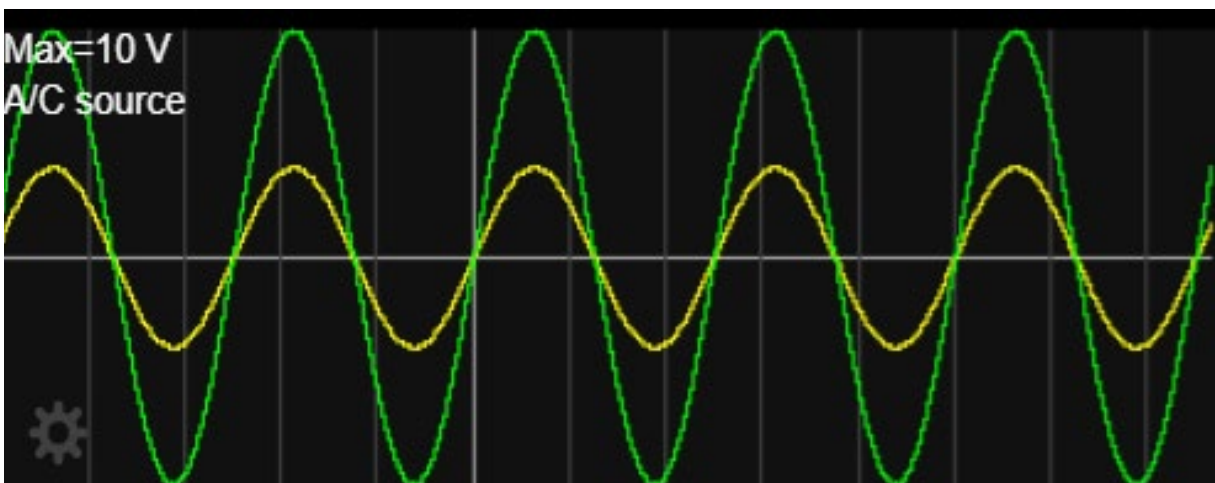

Input-2




Output

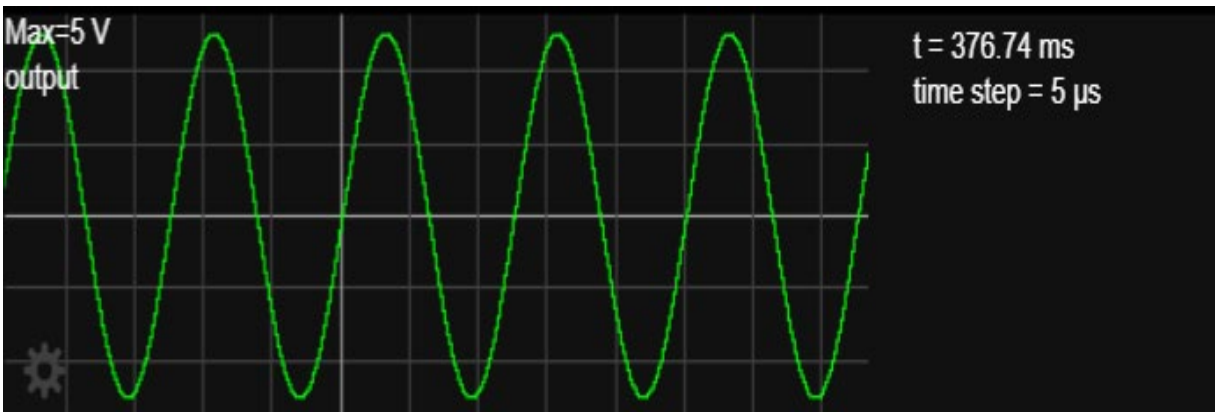

[Link](#)

5.Integrator

Circuit Diagram

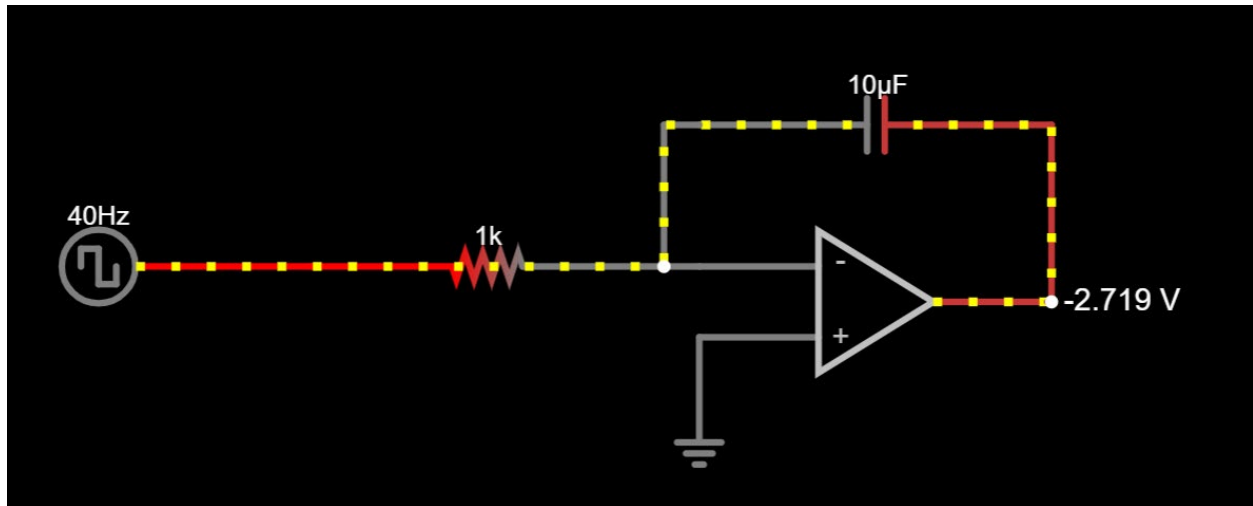

Input






[Link](#)

6.Differentiator


Circuit Diagram

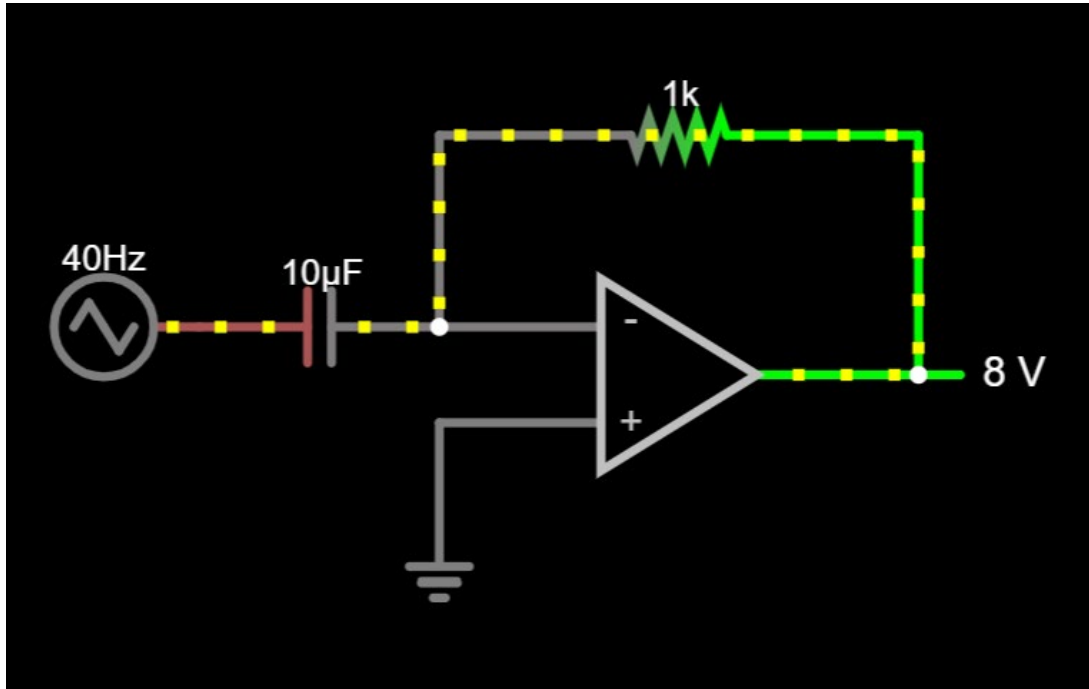

Input




Output

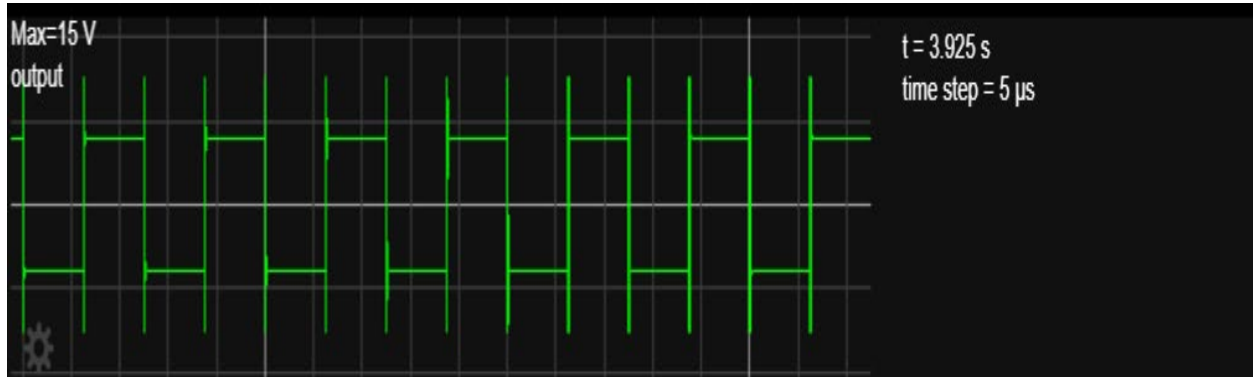

[Link](#)

7.INVERTING COMPARATOR


Circuit Diagram :-

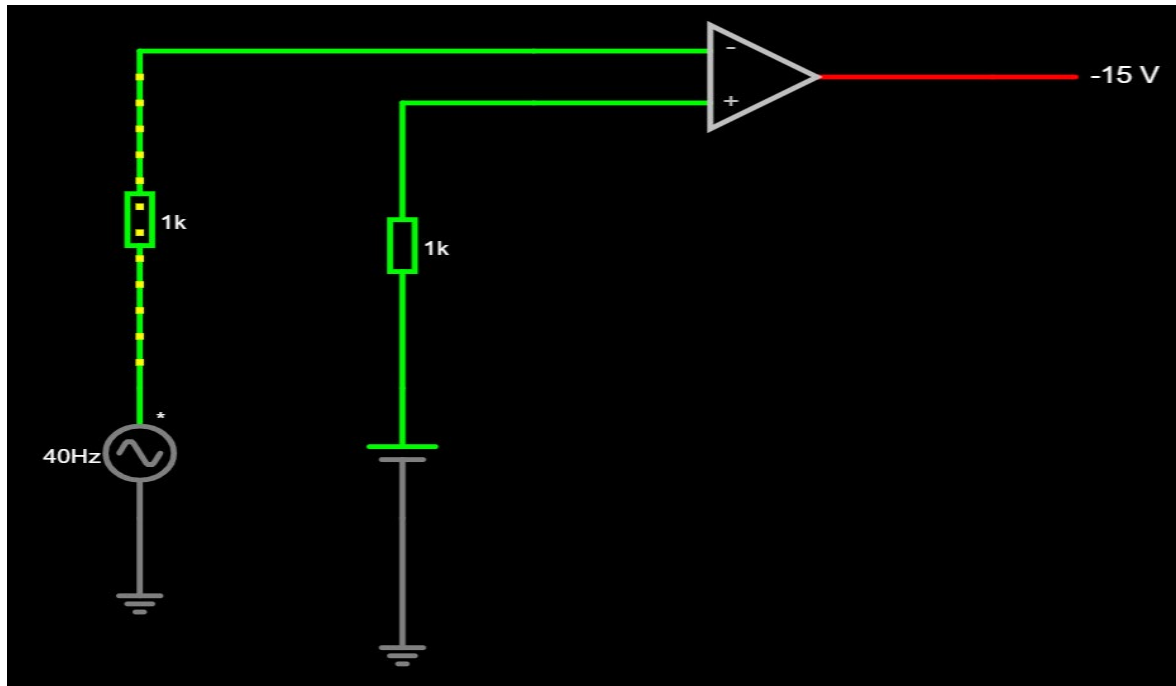

Input :-




Output :-

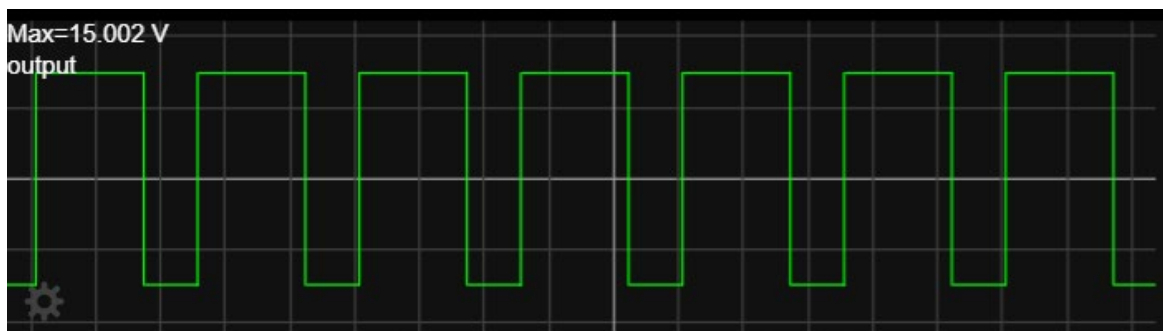


[LINK](#)

8. NON-INVERTING COMPARATOR


CIRCUIT DIAGRAM: -

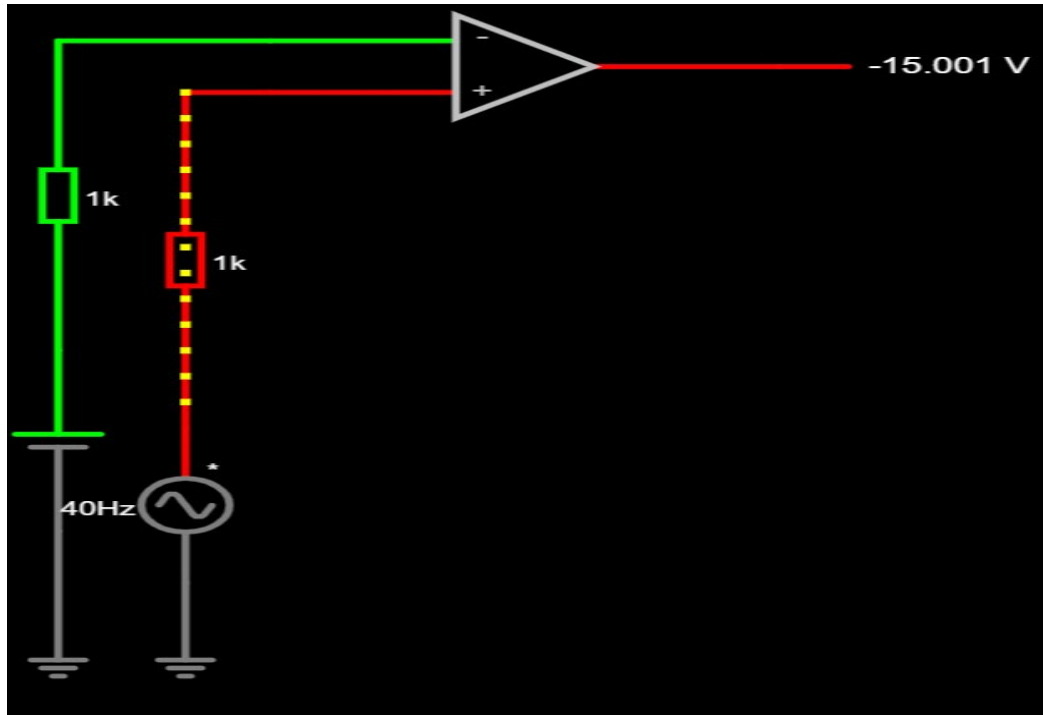

INPUT: -

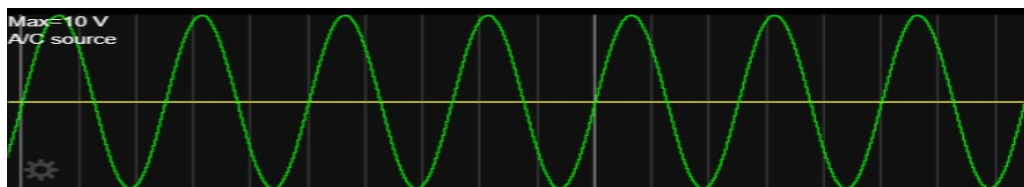


OUTPUT: -

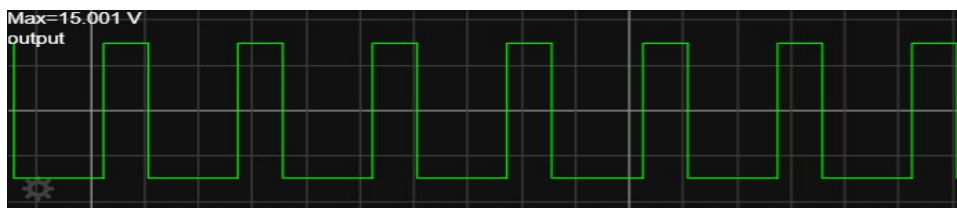


[LINK](#)

9.ZERO-CROSSING DETECTOR

CIRCUIT DIAGRAM: -

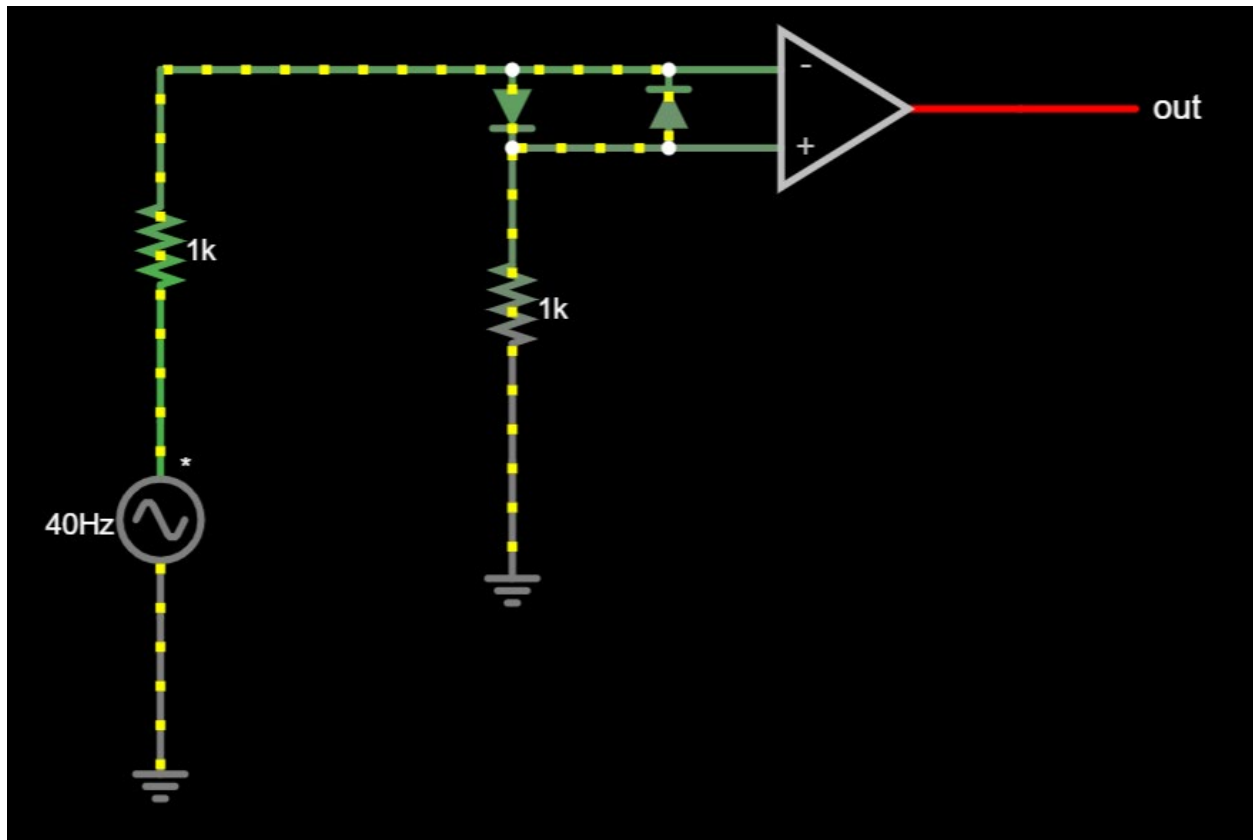

INPUT: -

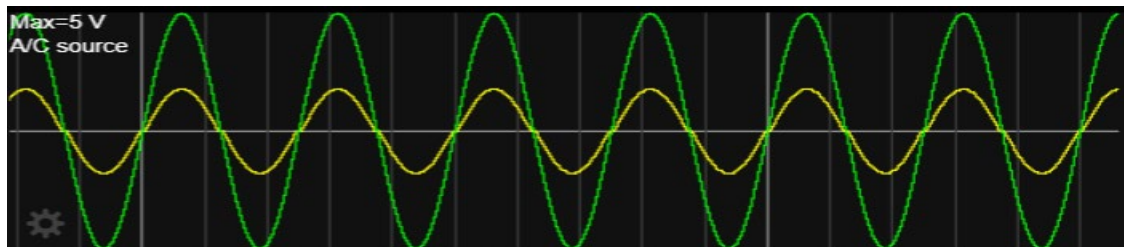

OUTPUT: -




[LINK](#)

10) Schmitt Trigger

a) Ideal Op-AMP ([LINK](#))

Picture: -

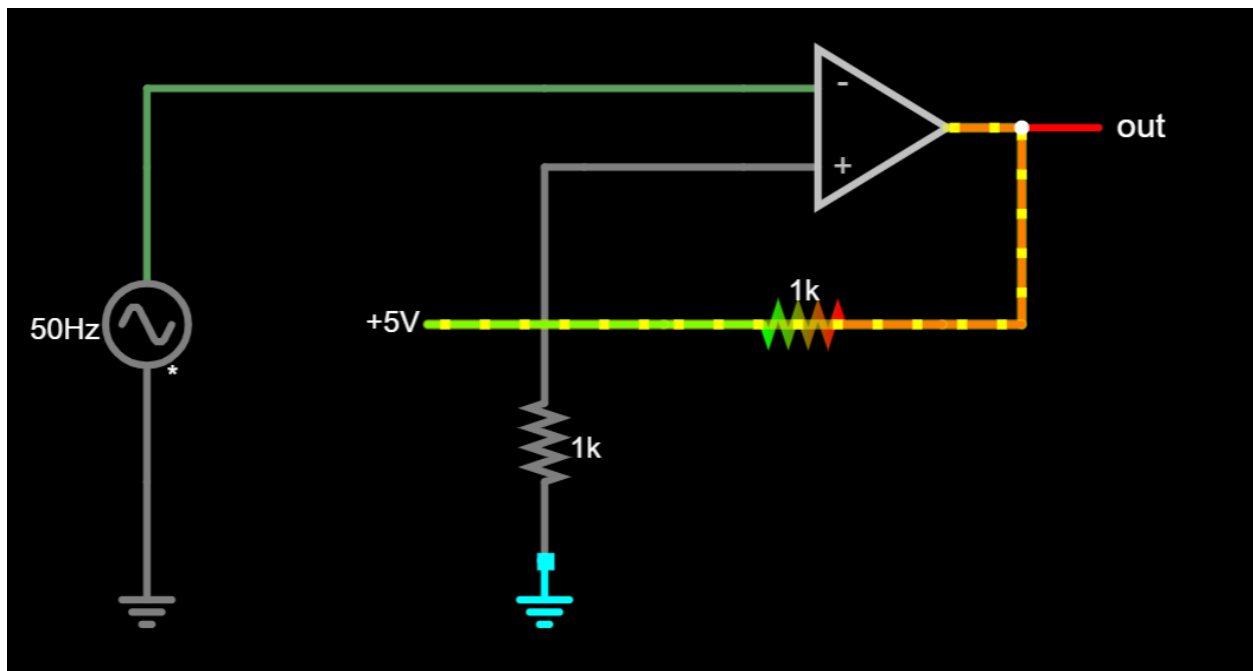

Input:




Output:



b) Non-Ideal Op-AMP ([LINK](#))


Circuit:

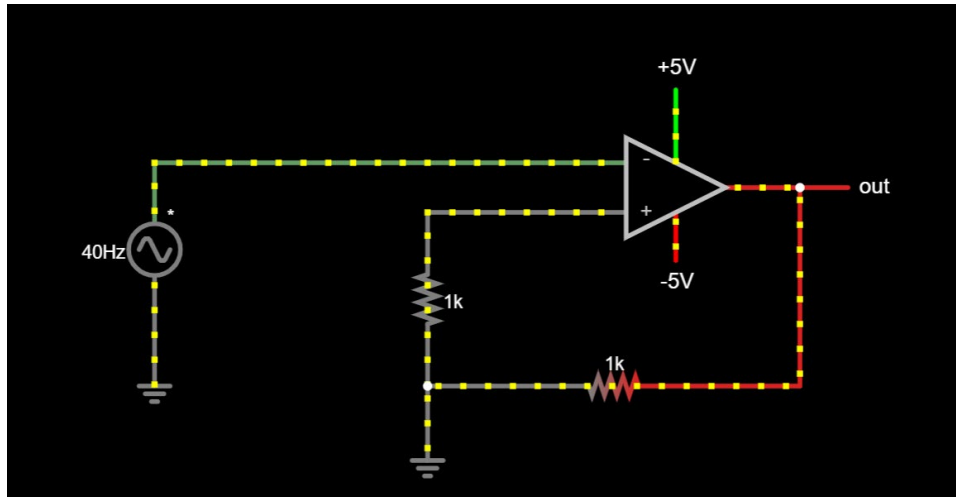

Input waveform: -




Output Waveform: -

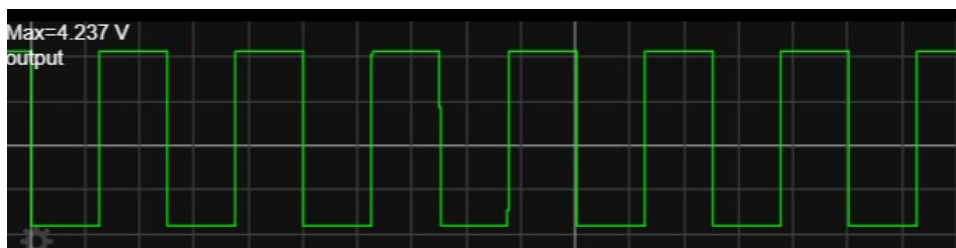


11) Astable Multivibrator ([Link](#))

a) Ideal Op-AMP

Circuit : -

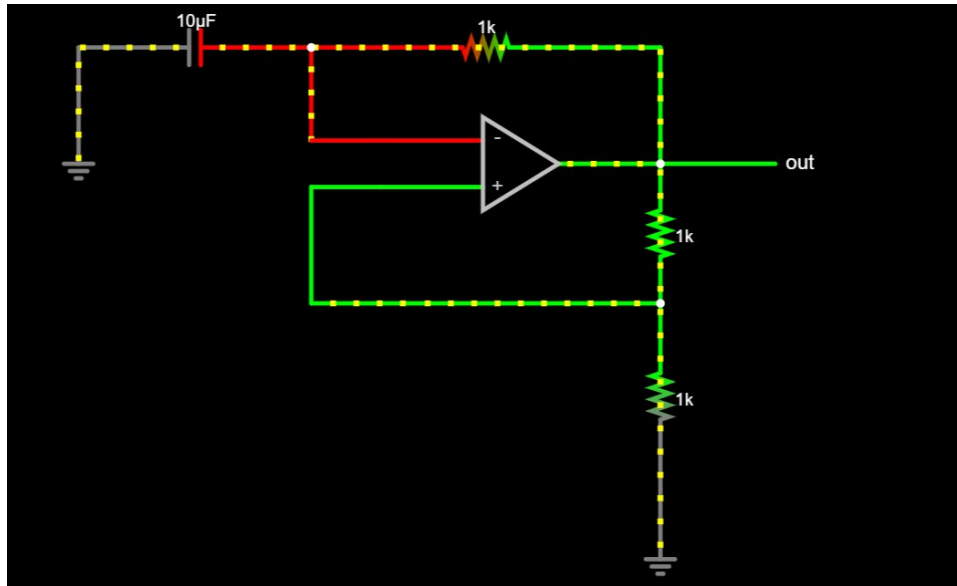

Input waveform: -

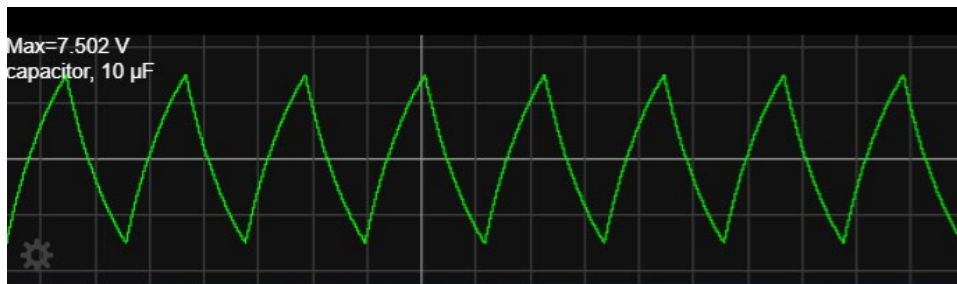


Output Waveform: -




b) Non-Ideal Op-AMP ([LINK](#))


Circuit:

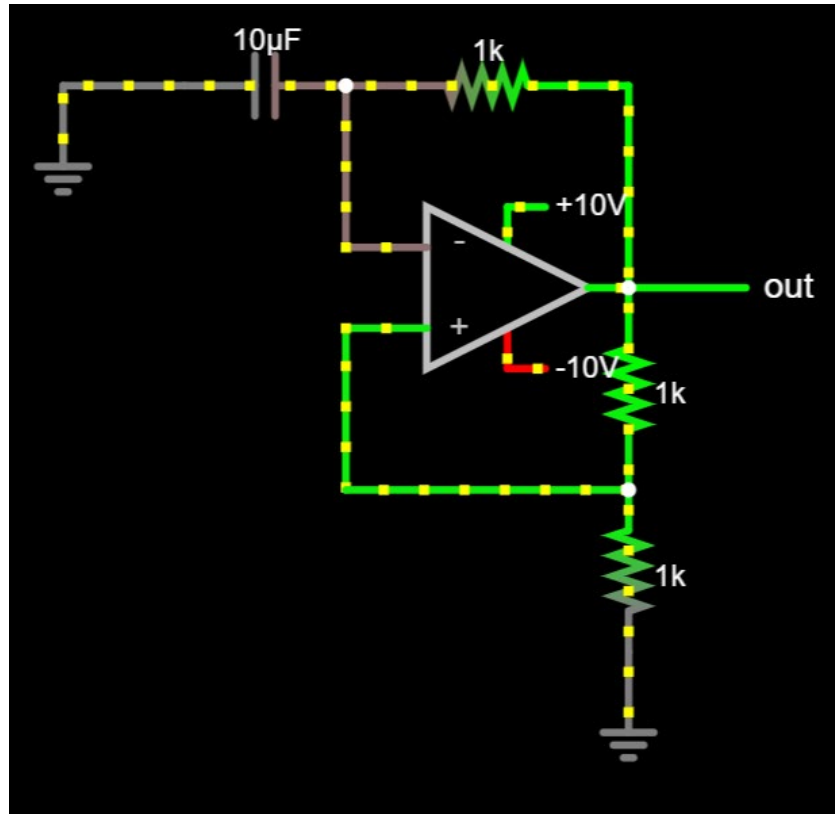

Input:

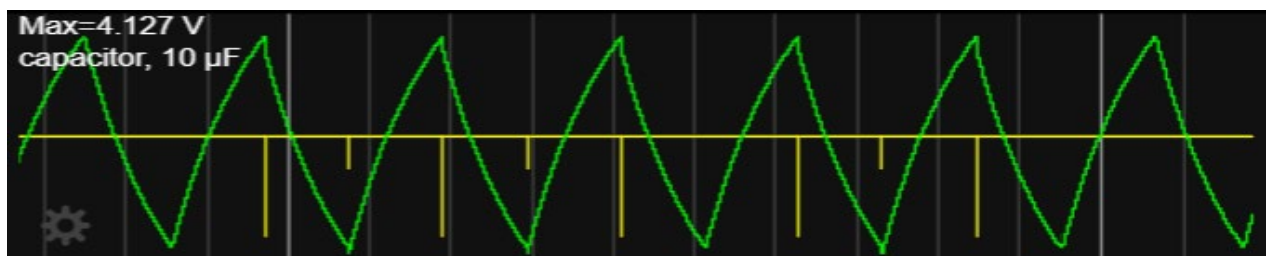


Output:

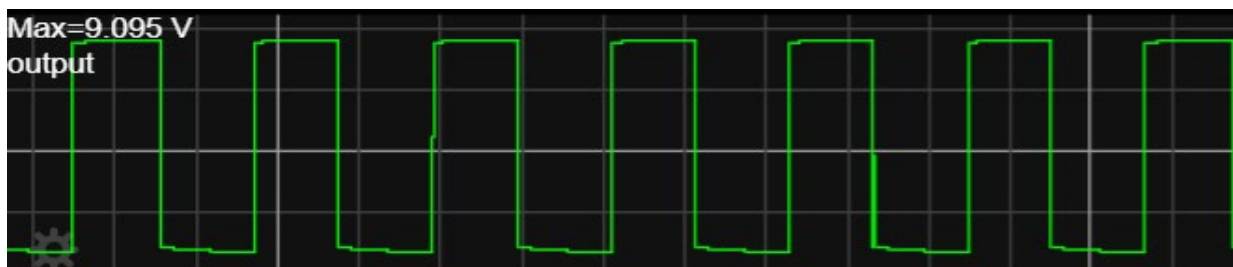


12) Resistive-ladder DAC([Link](#))

Picture: -

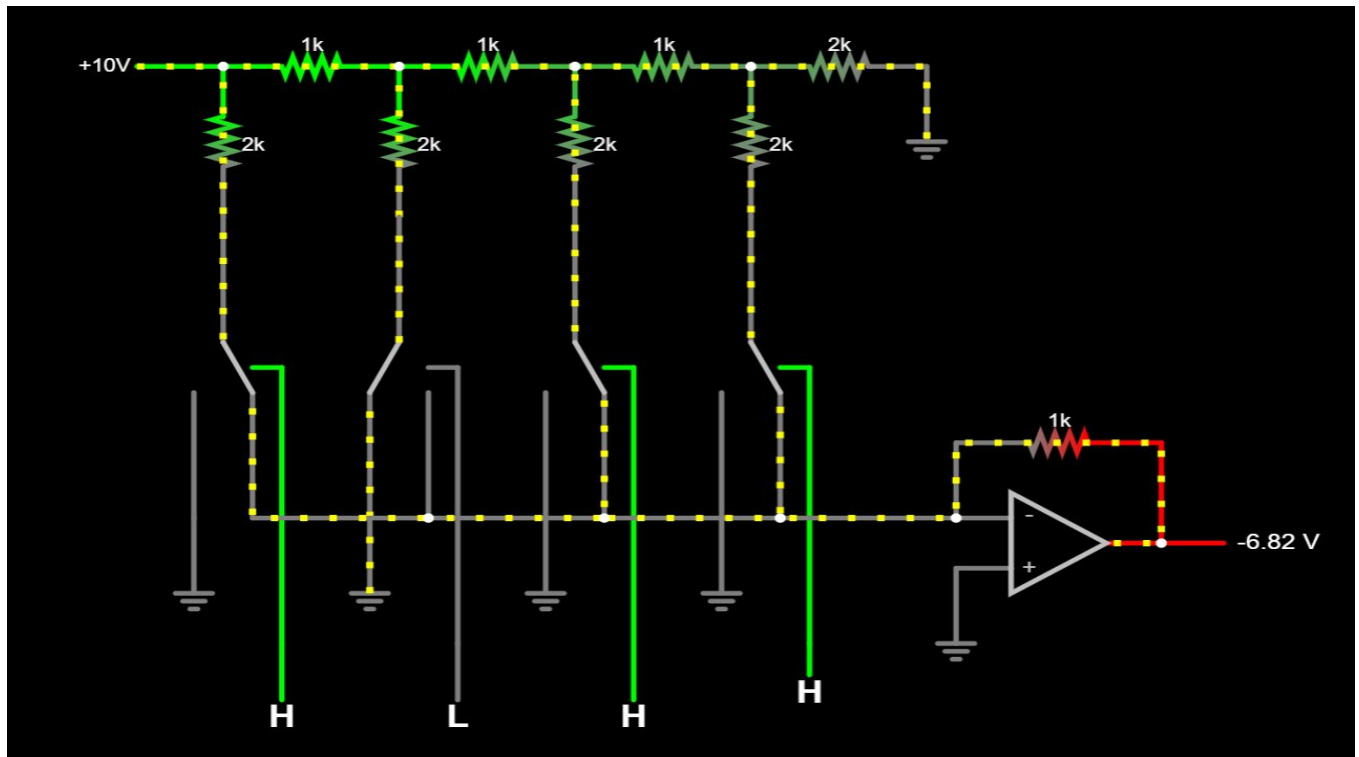

INPUT:

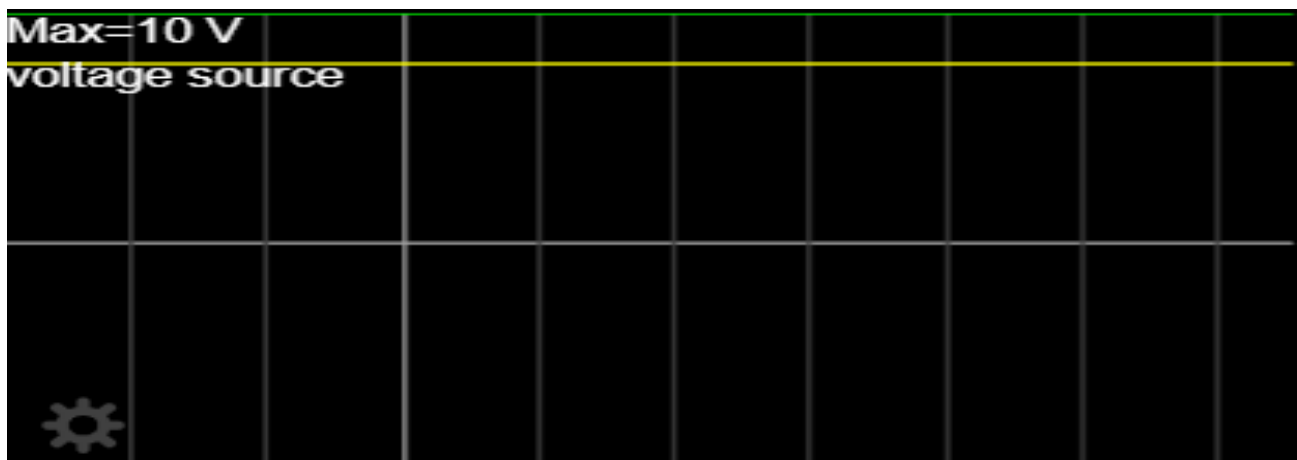

OUTPUT:

