

19AIE104 Introduction to Electrical Engineering

TEAM 11 BATCH A

GROUP MEMBERS:

1.VIKHYAT BANSAL[AIEA.1007359]

2.VIGNESH M

3. YARRAM SRI SATHWIK REDDY[AIEA.1038833]


4. MOHIT SASANK REDDY MARREDDY [AIEA.1011669]

•Q1 --Apply A single-phase inductor coil (non-ideal, not purely inductive) used in an SMPS (UPS) connected to a supply of 220 V at 60 Hz, takes a current of 4 A. The coil dissipates 750 W.

Calculate

1. The resistance and the inductance of the coil.
- 2.The power factor of the coil.
- 3.Considering the resistive power loss, estimate the efficiency of the inductor coil.

2.

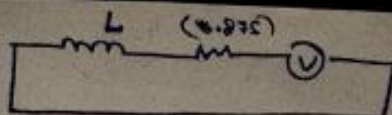

Voltage 220 V

frequency 60 Hz

Current \Rightarrow 4 A

Real (output power) \Rightarrow 750 W

1.

$$V = iZ$$

$$220 = 4\sqrt{R^2 + X_L^2}$$

$$55 = \sqrt{R^2 + X_L^2} \quad \text{--- (1)}$$

Calculating resistance using power dissipated

$$750 = i^2 R$$

$$750 = (4)^2 R$$

$$\boxed{46.875 = R}$$

Now we know from (1)

$$(55)^2 = (46.875)^2 + (X_L)^2$$

$$3025 = 2197.265 + (X_L)^2$$

$$\sqrt{827.735} = X_L$$

$$\boxed{28.77 = X_L}$$

$$X_L = 2\pi f(L)$$

$$28.77 = 120\pi(L)$$

$$\boxed{L = 0.076 \text{ H}}$$

2. we know power factor $\Rightarrow \frac{R}{Z} (\cos\phi)$

or

$\Rightarrow \frac{\text{True power}}{\text{Apparent Power}}$

$$\Rightarrow \frac{46.875}{55} \quad \text{or} \quad \frac{750}{880} \Rightarrow 0.85227$$

Efficiency @ Efficiency $\Rightarrow \frac{\text{True Power}}{\text{Apparent Power}} * 100$

$$\Rightarrow \frac{750}{880} * 100$$

$$\Rightarrow 85.227$$

•Q2 --Calculate and Analyse If the inductor coil mentioned in Q1 is used in a 230 V, 50 Hz power supply, analyse and comment on the following:

1.Change in power loss

2.Variation in power factor and impedances

3.The change in efficiency with the new power supply

4.The power factor and efficiency if a capacitor of $100\mu F$ is connected in series with the inductor coil.

Q2 Details already mentioned in Q1
 old voltage $\Rightarrow 220V$ New Voltage $\Rightarrow 230V$
 old freq $\Rightarrow 60Hz$ New freq $\Rightarrow 50Hz$
 Current ? Resistance $\Rightarrow 46.875 \Omega$
 $X_L \Rightarrow ?$ Inductance $\Rightarrow 0.076H$
 $Z \Rightarrow ?$ (i) $Z = 280$

firstly let us calculate impedance

$$X_L = 2\pi f(L)$$

$$= 100\pi(0.076)$$

$$= 314\left(\frac{76}{1000}\right)$$

$$= 23.864$$

$$Z = \sqrt{(46.875)^2 + (23.864)^2}$$

$$Z = \sqrt{2197.26 + 569.49}$$

$$Z = 52.59$$

using this impedance and voltage we get current

$$4.37A = \text{current}$$

1. Power loss using i^2R we get

$$(4.37)^2 (46.875)$$


$$\Rightarrow 895.16 W$$

so for change in power loss we will do

New - Old

$$\Rightarrow 895.16 - 750.00$$

$$\Rightarrow 145.16 W$$

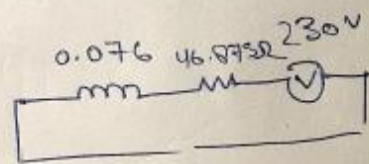

2. Power factor $\Rightarrow R/Z \Rightarrow \frac{46.875}{52.59}$

$$\Rightarrow 0.8912$$

Variation \Rightarrow New - old

$$\Rightarrow 0.8912 - 0.8522$$

$$\Rightarrow 0.039$$

Q2 3.

Efficiency

New Efficiency

New Apparent Power $\Rightarrow 1005 \text{ W}$

New Power Dissipated $\Rightarrow 895.16 \text{ W}$

$$\text{Efficiency} \Rightarrow \frac{895.16}{1005} * 100$$

$$\Rightarrow 0.89 * 100$$

$$\Rightarrow 89\% \text{ (Approx)}$$

4. New circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$R = 46.875 \Omega$$

$$L = 0.076 \text{ H}$$

$$C = 100 \times 10^{-6} \text{ F}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi(10^{-6} \times 100)}$$


$$= \frac{10^2}{3.14} = 31.84$$

$$X_L = 23.864$$

$$X_C > X_L$$

It means overall circuit have leading current
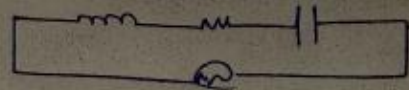
$$\text{Power factor} = \frac{R}{Z} = \frac{46.875}{47.54} = 0.986$$



$$Z = (\sqrt{2197.26 + 63.68})$$

$$Z = 47.54$$

$$230 = (47.54)(I)$$

$$I = 4.83 \text{ A}$$

Q2 4

Efficiency

Apparent Power using VI is 1112.74W
True Power using (i^2R) is 1093.54W

$$\text{Efficiency} \Rightarrow \frac{1093.54}{1112.74} * 100$$

$$\Rightarrow 0.9827 * 100$$

$$\Rightarrow 98.27 \%$$

•Q3 --Calculate and Analyse Consider a parallel RLC circuit composed of 100Ω , $100\mu F$ and $75mH$ being supplied by a 240 V, 50 Hz power supply.

Calculate and compare the system to the one mentioned in Q2.4.

1.Impedances,

2.Apparent power, active power, power factor, and reactive power.

3.Variation in power factor and impedances

4.The change in efficiency with the new power supply

5.The power factor and efficiency if a capacitor of $100\mu F$ is connected in series with the inductor coil

(i) Given,

$$f = 50 \text{ Hz}, R = 100 \Omega, L = 75 \times 10^{-3} \text{ H}$$

$$C = 100 \times 10^{-6} \text{ F}$$

$$\text{Now, } X_L = 2\pi f \cdot L$$

$$= 2 \times \pi \times 50 \times 75 \times 10^{-3}$$

$$= 23.56$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times \pi \times (50) \times (100 \times 10^{-6})} = 31.83$$

$$\text{Now, Impedance (Z)} = \frac{1}{\sqrt{\frac{1}{R^2} + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}}$$

$$= \frac{1}{\sqrt{\frac{1}{(100)^2} + \left(\frac{1}{23.56} - \frac{1}{31.83}\right)^2}}$$

$$= 67.56$$

3)

(2) (i) Apparent Power $= I^2 \times Z$
 $= (2.4)^2 \times 100 = 576 \text{ VA}$

$$I = \frac{V}{R} = \frac{240}{100} = 2.4$$

(ii) Reactive Power:-

$$X_T = X_L - X_C$$

$$X_T = 0.075$$

$$\begin{aligned} \text{Reactive Power} &= I^2 X_T \\ &= (5.76)(0.075) \\ &= 0.432 \text{ VAR} \end{aligned}$$

(iii) Power factor:-

$$\begin{aligned} \text{Power factor } (\cos \phi) &= \frac{I^2 R}{I^2 Z} = \frac{R}{Z} = \frac{100}{167.56} \\ &= 0.6756 \end{aligned}$$

3)

(3) Variation in Power factor:-

$$= 0.815 - 0.6586$$

$$= 0.1564$$

Variation in impedance:

$$= 167.56 - 57.51$$

$$= 110.06$$

$$4) \quad \text{efficiency} = \left(\frac{\text{output power}}{\text{input power}} \right) \times 100$$

$$\text{output Power} = \text{input Power} - \text{Power dissipated}$$

$$= \frac{240 \left(\frac{240}{67.56} \right) - \left(\frac{240}{67.56} \right)^2 \times (67.56)}{\left(\frac{240}{67.56} \right)^2}$$

$$\text{efficiency} = 0.0128 \times 100 = 1.28\%$$