

21AIE113- INTRODUCTION TO ELECTRONICS

Group Assignment 1

Submission Date: 03/04/2022,11.59 PM

Submission link: [Assignment 1](#)

Answer all Questions

One submission per group

Submission format – doc,pdf

1. Perform the experiment of Forward Bias and Reverse Bias of a PN junction silicon diode in Falstad circuit simulator.
 - a) Explain the theory behind the experiment
 - b) Draw the circuit diagrams, mention the components used, and state the procedure of the experiment.
 - c) Plot the V-I characteristics, mark the cut-in voltage, and calculate the static and dynamic resistance in the case of forward bias. Write down the inference from the VI characteristics.
2. Write a Matlab program to calculate the current flowing through a diode during forward bias. (Hint: Shockley's equation and consider n as 1).
3. The reverse saturation current of a diode at 25 deg Celsius is 10pA. Plot the forward characteristic of the diode at the 0 degree Celsius and 100 degree Celsius. Write down the inference from the plot.

Hint: The expression for the reverse saturation current is as a function of temperature is

$$I_s(T_2) = I_s(T_1)e^{[k_s(T_2-T_1)]}$$

where $k_s = 0.072 / \text{deg Celsius}$. T_1 and T_2 are two different temperatures